

DLDCALab 3: Verilog

Week 4

August 21, 2026

Introduction

This week we continue our exploration of Verilog by designing larger, more realistic systems. We will practice breaking a problem into smaller, well-defined components and wiring them together – a core skill in hardware design.

We will write **Finite State Machines (FSMs)**: circuits that maintain state and transition between well-defined modes of operation based on inputs. FSMs appear everywhere in real hardware – traffic controllers, communication protocols, CPU control units. We will design one together, walking through how to identify states, transitions, timing variables, and outputs, before writing the Verilog.

Later in the lab, we briefly touch upon two more powerful Verilog features: **parametric modules**, which let you write a single module that works at any bit-width, and **generate blocks with genvar**, which let you instantiate and wire up hardware structures in a loop. **These are not assessed in this lab’s graded component but will be useful going forward.**

The labexam is a slightly more advanced problem based on writing combinational logic and FSMs.

Necessary tools

We shall be using `icarus-verilog` (or) `iverilog` in order to compile verilog HDL (Hardware Description Language). To visualize waveforms we shall use the VS Code extension ‘Vaporview’. Before starting the lab, ensure that both tools are installed in your system. This can be verified by running the following:

```
$ iverilog
iverilog: no source files.

Usage: iverilog [-EiRSuvV] [-B base] [-c cmdfile|-f cmdfile]
               [-g1995|-g2001|-g2005|-g2005-sv|-g2009|-g2012] [-g<feature>]
               [-D macro[=defn]] [-I includedir] [-L moduledir]
               [-M [mode=]depfile] [-m module]
               [-N file] [-o filename] [-p flag=value]
               [-s topmodule] [-t target] [-T min|typ|max]
               [-W class] [-y dir] [-Y suf] [-l file] source_file(s)
```

See the man page for details.

Structure of submission/templates

Submission format:

```
your-roll-no/  
|- task1/  
    |- traffic_fsm.v (TODO)  
    |- tb_task1.v  
|- task2/  
    |- crc.v (TODO)  
    |- tb_task2.v  
|- labexam/  
    |- jean_grey_decoder.v (TODO)  
    |- tb_labexam.v
```

The folder structure of the expected submission for this lab is given above. We expect this folder to be compressed into a tarball with the naming convention of `your-roll-no.tar.gz`. The command given below can be used to do the same

```
$ tar -cvzf your-roll-no.tar.gz your-roll-no/
```

Alternatively, use the provided `build-archive.sh` script to help you do the same.

```
# cd into the <NN>_inlab folder, NOT the inner folder  
$ ./build-archive.sh
```

Tasks

Task 1: Traffic Light Controller – Help Bhavesh!

Bhavesh wants to cross JVLR road, but traffic is horrible. Help him build a traffic light controller from scratch by implementing three sub-modules and wiring them together in a top-level module.

This is the same system designed in the slides. The goal is to implement it yourself from scratch. Try to write it top-down: wire the three modules together into a working system, then implement each and test.

Specification

The circuit continuously cycles `GREEN` $\rightarrow$ `YELLOW` $\rightarrow$ `RED` $\rightarrow$ `GREEN`, driven by a 1Hz tick signal. Resetting (`rst_n` active-low) forces the state to `GREEN` with `remaining` = 25.

State Encodings: `GREEN` = 2'b00, `YELLOW` = 2'b01, `RED` = 2'b10.

The pedestrian button (`ped_button`) modifies the duration of the current phase and may also be remembered for a later phase using the latched signal `ped_request`.

State	Normal duration	Duration with request
GREEN	25 ticks	Shortened by 10 ticks on button press 5 ticks 40 ticks if <code>ped_request</code> is latched / <code>ped_button</code> is pressed
YELLOW	5 ticks	
RED	30 ticks	

A pedestrian button press during **GREEN** immediately shortens the remaining **GREEN** duration by 10 ticks, with a minimum remaining duration of 1 tick, and is remembered. A press during **RED** immediately extends its remaining duration by 10 ticks. A press during **YELLOW** cannot modify the current duration, but is remembered so that the upcoming **RED** phase starts with duration 40 instead of 30.

Pedestrian Latching

- **Set:** A high `ped_button` pulse sets `ped_request = 1`.
- **Persistence:** The request remains latched after the button is released and is used when entering **RED**.
- **Reset:** `ped_request` is cleared during the **RED** → **GREEN** transition.
- **One-shot modification:** The instantaneous button modifier is enabled only when `ped_button && !ped_request`. This prevents a held button from repeatedly shrinking or extending the duration.

Understanding remaining — Datapath

The `remaining` value (exposed as `duration_out` in the top module) tracks time left in the current state.

- **Initialization:** On reset, `remaining` is initialized to 25.
- **Countdown:** On every `tick_1hz`, if `remaining > 1`, it decrements by 1.
- **Transition:** When `remaining = 1` on a tick, the controller transitions to the next state and loads that state's starting duration.
- **Starting durations:** **GREEN**=25, **YELLOW**=5, and **RED**=30 normally, or 40 when `ped_request=1`.

Module Structure & Data Flow

Wire three sub-modules inside the top-level `bhavesht_traffic_light`:

- `traffic_fsm` (control/sequential): Owns the registers `current_state`, `remaining`, and `ped_request`. It sequences the states and latches values computed by the datapath.
- `duration_datapath` (combinational): Computes `remaining_next` and `do_transition` from the current state, remaining duration, tick, and pedestrian inputs.
- `output_decoder` (combinational): Takes `current_state` and produces `red`, `green`, and `yellow`.

`duration_datapath`

The datapath is purely combinational and owns no registers. Its job is to calculate what should happen to `remaining` before the control logic latches the result.

It first processes the normal 1Hz update. If `tick_1hz` is high and `remaining > 1`, it computes `remaining_next = remaining - 1`. If `remaining = 1`, it asserts `do_transition` and loads the duration of `next_state`.

It then applies the instantaneous pedestrian modifier. If `ped_button && !ped_request && !do_transition` is true, then:

- During **GREEN**: `remaining_next` is reduced by 10, with a minimum value of 1.

- During RED: `remaining_next` is increased by 10.
- During YELLOW: no immediate duration modification is made; the button is instead latched by the control logic and affects the subsequent RED duration.

Note: The `!do_transition` condition ensures that a pedestrian button present on a transition tick is ignored (refer to slides).

Implementation Notes

Fill in the TODOs in the provided skeleton file.

Testbench and Monitor

The testbench runs unit tests on `duration_datapath` and `output_decoder`, followed by full system integration tests. You can read the output to understand what is being tested, and code and comments to see the exact details — you may write your own tests!

Monitor output line format:

```
t= 150 | tick=1 | state=GREEN remaining= 25 | R=0 G=1 Y=0 | ped=0 | request=0
```

Testing Tips:

- View the `.vcd` output for a quick sanity check.
- Reduce durations (e.g. `8'd5`, `8'd3`) while testing to get a much shorter trace.
- Check `[ASSERT]` status lines (PASS/FAIL) for quick validation.
- Watch `remaining` count down and verify that a transition occurs when it reaches 1 on a tick.
- Confirm that a button press during GREEN immediately shrinks the remaining duration by 10, with a floor of 1.
- Confirm that a button press during YELLOW is remembered and causes the next RED phase to start at 40 ticks.
- Confirm that a button press during RED immediately extends the remaining duration by 10.
- Confirm that `ped_request` latches on a button press and clears on the RED → GREEN transition.
- Remove `clk` from `$monitor` output to reduce the number of output lines.

Note the `make` command will run the testbench and diff with expected output, and print a final Output `matches/does not match` message.:

```
$ make task1
```

Task 2: CRC Engine

CRC (Cyclic Redundancy Check) is used by real protocols such as Ethernet, USB, and HDMI to verify data integrity. The sender computes a checksum over a stream of bits and appends it to the data. The receiver recomputes the checksum and compares the two values.

You will implement a CRC engine in three parts.

See the **Testing** section for how to verify your CRC output against the provided Python script.

The Algorithm

CRC is computed serially, one bit at a time. One iteration is:

```
feedback = crc[MSB] XOR incoming_bit

if feedback == 1:
    crc = (crc << 1) XOR POLY
else:
    crc = (crc << 1)
```

Start with `crc = INIT = ff...ff` (all 1s) and feed the message bits through the loop, MSB first. The final `crc` value is the checksum.

Recall: For an N -bit register, left-shift and append 0 using `{crc[N-2:0], 1'b0}`.

Implementing CRC-8 (Fixed Width)

Implement the following two CRC-8 modules:

width = 8 bits, polynomial = 8'hD5, initial value = 8'hFF.

crc8_update (combinational)

Implement one iteration of the CRC algorithm. The module takes the current CRC value and one input bit, and produces the next CRC value.

Use only **assign** statements.

```
module crc8_update (
    input  [7:0] crc_in,
    input      data_bit,
    output [7:0] crc_out
);
```

crc8_serial (sequential)

Accumulate the CRC over a stream of bits. On each clock edge where `valid` is high, feed `data_bit` through `crc8_update` and store the result in the CRC register.

Reset the register to `8'hFF` when `rst` is asserted. The `crc` output must always reflect the current register value.

```

module crc8_serial (
    input      clk, rst,
    input      data_bit,
    input      valid,
    input      done,
    output [7:0] crc
);

```

You must instantiate `crc8_update` inside this module and connect it to the CRC register.

Food for thought

Can we extend this algorithm to arbitrary widths of CRC width? What about processing bits in parallel? We will explore these later!

Testing

Manual verification

Run the verifier in interactive mode:

```
python3 task2/verifier.py
```

It will prompt you for the message, width, polynomial, and initial value, then print the expected CRC.

Automated testing

Use the Makefile:

```
$ make task2
```

This compiles your code and produces `task2.vvp`, then runs it once to show debug output. You can open the resulting `task2.vcd` in VaporView.

Finally, it runs the verifier in autograde mode:

```
python3 task2/verifier.py --autograde
```

A successful run will look like:

```

=== RUNNING CRC_VERIFIER.PY ===

Running task2.vvp...

TEST 1: PASS (MSG=AB, WIDTH=8, POLY=D5, INIT=FF, CRC=31)
...

3/3 CRC tests passed.

```

Lab Exam: Jean Grey's Secret Channel

Jean Grey is intercepting a serial data stream and injecting **invalid triples** — 3-bit patterns that should never appear in clean data. Your job is to build a clocked sequential circuit that reads the stream **3 bits at a time**, decodes valid triples into 2-bit outputs, and uncovers the secret message Jean hides in her injections.

All resets are **active-high** and **asynchronous**: use always `@(posedge clk or posedge rst)`.

Note: In case of any ambiguity the order of resolution is: common clarifications shared by TAs > testbench output and code comments > the problem statement pdf.

Encoding Scheme

Only 4 of the 8 possible triples are valid:

Triple (<i>ABC</i>)	Decoded (<i>XY</i>)	Valid (<i>V</i>)
0 0 0	- -	0
0 0 1	0 0	1
0 1 0	0 1	1
0 1 1	1 0	1
1 0 0	- -	0
1 0 1	1 1	1
1 1 0	- -	0
1 1 1	- -	0

The triples 000, 100, 110, 111 are **invalid**. Any invalid triple was placed there by Jean.

How the System Works

The circuit receives a 4-bit **count** and a **start** signal. When **start** goes high, it reads exactly **count valid** triples from the input, one per clock. Each valid triple is decoded and output as a 2-bit **pair**.

When an **invalid triple** is seen:

- It is **ignored** — does not count toward **count**, produces no output.
- The **very next triple** is Jean's secret — it is XORed into a running **secret** accumulator.
- Normal reading then resumes.

When all **count** valid triples are read, **done** is asserted for one cycle.

Note: Some code will be provided as boilerplate / helper modules to you do NOT edit them.

Part (a) — Combinational Decode Logic

Before writing any Verilog, derive minimal SOP/POS expressions using Karnaugh maps for:

- **V** — 1 if the triple is valid
- **X** — MSB of decoded output
- **Y** — LSB of decoded output

Note: For X and Y, invalid triples are don't-cares. This can help you write simpler POS/SOP expressions.

Module 1: triple_decoder

Purely combinational. Use **only** assign statements — no if, else, or case. Some reasonable simplification is expected; writing the absolute smallest SOP/POS is not needed.

```
module triple_decoder (
    input  [2:0] triple,
    output      valid,
    output [1:0] pair
);
    wire A = triple[2];
    wire B = triple[1];
    wire C = triple[0];

    assign valid  = /* V from your K-map */;
    assign pair[1] = /* X from your K-map */;
    assign pair[0] = /* Y from your K-map */;
endmodule
```

Module 2: secret_accumulator (provided – DO NOT MODIFY)

Do not modify this. It XORs the incoming triple into secret whenever capture is high for one posedge.

```
module secret_accumulator (
    input      clk, rst,
    input [2:0] triple,
    input      capture,
    output reg [2:0] secret
);
    always @(posedge clk or posedge rst) begin
        if (rst) secret <= 3'b000;
        else if (capture) secret <= secret ^ triple;
    end
endmodule
```

Module 3: jean_grey_decoder

Top-level module. Instantiates triple_decoder and secret_accumulator, and contains the FSM.

```
module jean_grey_decoder (
    input      clk, rst, start,
    input [3:0] count,
    input [2:0] triple,
    output reg [1:0] pair,
    output reg      valid_out,
    output [2:0] secret,
    output reg      secret_out,
    output reg      done
);
```


Note: `secret` is output (a wire), wired directly from `secret_accumulator`'s output port — not driven by the FSM.

Declare the following and connect all ports:

```
wire      is_triple_valid;
wire [1:0] triple_pair;
/*reg/wire      capture*/;

triple_decoder td ( /* connect ports */ );
secret_accumulator sa ( /* connect ports */ );
```

Note: Figure out how to correctly define and set value to capture based on intended behaviour.

FSM States

```
localparam IDLE      = 2'b00;
localparam READ      = 2'b01;
localparam INTERCEPT = 2'b10;
localparam DONE      = 2'b11;

reg [1:0] state;
reg [3:0] remaining;
```

Allowed Transitions

IDLE	-> IDLE	when start is low
IDLE	-> READ	when start is high; set remaining <- count
READ	-> READ	consume valid triple, when remaining > 1
READ	-> DONE	consume valid triple, when remaining == 1
READ	-> INTERCEPT	consume invalid triple; do NOT decrement remaining
INTERCEPT	-> READ	always happens
DONE	-> IDLE	always happens

State Behaviour

IDLE: Hold all outputs at 0. Wait for `start`.

READ: Check `is_triple_valid` each cycle.

- If valid: drive `pair` and `valid_out`, decrement `remaining`, go to `DONE` if `remaining == 1`.
- If invalid: go to `INTERCEPT` — **do not decrement remaining**.

INTERCEPT: Assert `capture` for exactly this one cycle so `secret_accumulator` XORs the current triple in. Assert `secret_out`. Return to `READ`.

DONE: Assert `done` for one cycle. Return to `IDLE`.

Skeleton (IDLE and DONE given) – DO NOT MODIFY

```

always @(posedge clk or posedge rst) begin
    if (rst) begin
        state <= IDLE;
        remaining <= 0;
        pair <= 0; valid_out <= 0; done <= 0;
        secret_out <= 0;
    end else begin
        case (state)
            IDLE: begin
                pair <= 0;
                done <= 0; secret_out <= 0; valid_out <= 0;
                if (start) begin remaining <= count; state <= READ; end
            end
            READ:      begin /* your code */ end
            INTERCEPT: begin /* your code */ end
            DONE: begin done <= 1; state <= IDLE; end
        endcase
    end
end
end

```

Worked Example

Please understand output format correctly!

The table below shows what you would see in the testbench output. Each row is printed **1 ns after a rising clock edge**, so all signals shown are their values **after that clock edge**.

The **state** column is the FSM state after the edge, while **triple** is the input currently present at that time. The testbench uses this same convention when printing its output.

Assume posedge occurs at time 5, 15, etc.

For example: at the rising edge at **t=45**, the module is in **READ** and sees the input **triple=010**. This results in a transition to **READ** as shown on **t=46** from **READ** as shown on **t=36**.

```

// Before the rising edge at t=35:
count = 4'b0100; start = 1; triple = 3'b000;
// After the rising edge at t=35:
start = 0;

```

Time	State	triple	pair	valid_out	secret	secret_out	done
6	IDLE	000	00	0	000	0	0
16	IDLE	000	00	0	000	0	0
26	IDLE	000	00	0	000	0	0
36	READ	000	00	0	000	0	0
46	READ	010	01	1	000	0	0
56	INTERCEPT	110	00	0	000	0	0
66	READ	101	00	0	101	1	0
76	READ	001	00	1	101	0	0
86	READ	011	10	1	101	0	0
96	DONE	101	11	1	101	0	0
106	IDLE	101	00	0	101	0	1

Decoded pairs (valid cycles only): 01 00 10 11

Jean's secret: 3'b101